



NOTES

- 1) Use any P-Channel JFET with cutoff Vgs of about 2 volts. Fairchild J177 or NTE-489 or similar.
- Audio input signal should be "line level" approx. 1 volt peak to peak. That is roughly the level of the speaker output of a computer sound card or the earphone output of an iPod at medium-high volume.

IN-13 VU SOUND LEVEL METER WITH AUTOMATIC GAIN CONTROL

DANGER!!! HIGH VOLTAGES!!! USE AT YOUR OWN RISK